

Q. 33kV, 3 ϕ , 6.2MVA capacitor bank is to be installed at PCC where SC rating is 750MVA load is 20MW at 0.75pf. Harmonic spectrum is $I_{L5} = 4\%$, $I_{L7} = 10\%$, $I_{L11} = 8\%$, $I_{L13} = 4\%$. $Q = 100$. Design filter for 5th harmonic as for 11th there are freq 5 and 7 which will cause issue in ffn.

\Rightarrow

Tuning freq $\rightarrow 5^{\text{th}} \rightarrow 250\text{Hz}$

$$X_c = \frac{KV^2}{\text{MVA}_r} = \frac{(33/\sqrt{3})^2}{6.2/3} = -j175.64 \Omega$$

$$X_L = \frac{X_c}{n^2} = \frac{175.64}{25} = j7.025 \Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{100\pi (175.64)} = 1.81 \times 10^{-5} \text{F} = 18 \mu\text{F}$$

$$L = \frac{X_L}{100\pi} = \frac{7.025}{100\pi} = 22.36 \text{mH}$$


$$1) X_{\text{eff}} = |X_c - X_L| = 168.61 \Omega$$

$$2) I_{f1} = \frac{V_p}{|X_c - X_L|} = \frac{19.05 \times 10^3}{168.61} = 113 \text{A}$$

$$3) I_{\text{nom}} = \frac{V_p}{X_c} = \frac{19.05 \times 10^3}{175.64} = 108.46 \text{A}$$

$$4) V_{C1} = I_{f1} (X_{C1}) = 113 (175.64) = 19.84 \text{kV}$$
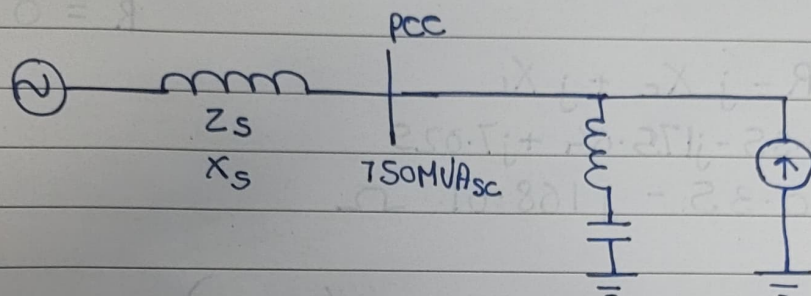
$$\begin{aligned}
 5) \text{ KVAR} &= V_{c1} \times I_{F1} \\
 &= 19.84 \times 10^3 \text{ (113)} \\
 &= 2241.92 \text{ KVAR} \\
 &= 2.241 \text{ MVar}
 \end{aligned}$$




$$X_s = \frac{KV^2}{MVA_{sc}} = \frac{(33/\sqrt{3})^2}{750/3} = j1.45 \Omega$$

$$L_s = \frac{X_s}{2\pi f} = \frac{1.45}{100\pi} = 4.615 \text{ mH}$$

$$f_{pi1} = \frac{1}{2\pi \sqrt{(L_s + L)C}} = \frac{1}{2\pi \sqrt{(22.36 + 4.61) \times 181 \times 10^{-8}}} = 4.55 \times 50$$

$$h_{pi1} = 4.55$$

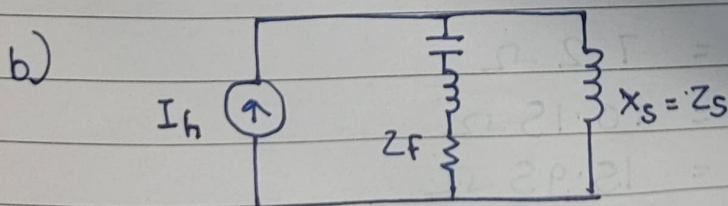

$$I_{L1} = \frac{P}{\sqrt{3} V_L \cos \phi} = \frac{20 \times 10^6}{\sqrt{3} (33 \times 10^3) 0.75} = 466.5 \text{ A}$$

$$I_{L5} = 186.61 \text{ A}$$

$$I_{L7} = 46.65 \text{ A}$$

$$I_{L11} = 37.32 \text{ A}$$

$$I_{L13} = 18.66 \text{ A}$$

$$Z_{fh} = R - j \frac{X_c}{h} + j h X_L$$

$$Z_{sh} = h X_s$$

$$Q = \frac{X_o}{R} = \frac{X_c/h}{R} = \frac{175.64}{R}$$

$$R = 0.35 \Omega$$

$$\begin{aligned} Z_{f1} &= R - j X_c + j X_L \\ &= 0.35 - j 175.64 + j 7.025 \\ &= 0.35 - j 168.61 \Omega \end{aligned}$$

$$\begin{aligned} Z_{fs} &= 0.35 - j 175.64 + j 5(7.025) \\ &= 0.35 - j 168.61 \Omega \end{aligned}$$

$$\begin{aligned} Z_{f7} &= 0.35 - \left(\frac{175.64}{7} \right) + j 7(7.025) \\ &= 0.35 + 24.08j \Omega \end{aligned}$$

$$\begin{aligned} Z_{f11} &= 0.35 - j \left(\frac{175.64}{11} \right) + j 11(7.025) \\ &= 0.35 + 61.30j \Omega \end{aligned}$$

$$\begin{aligned} Z_{f13} &= 0.35 - j \left(\frac{175.64}{13} \right) + j 13(7.025) \\ &= 0.35 + 77.81j \Omega \end{aligned}$$

$$Z_{s5} = 5(1.45) = 7.2 \Omega$$

$$Z_{s7} = 7(1.45) = 10.15 \Omega$$

$$Z_{s11} = 11(1.45) = 15.95 \Omega$$

$$Z_{s13} = 13(1.45) = 18.85 \Omega$$

	5	7	11	13
Z_f	0.35	24.08	61.3	77.81
Z_s	7.2	10.15	15.95	18.85

$$I_{fh} = \frac{Z_{sh}}{Z_{sh} + Z_{fh}} I_{Lh}$$

$$I_{sh} = \frac{Z_{fh}}{Z_{sh} + Z_{fh}} \times I_{Lh}$$

$$I_{fs} = \frac{7.2}{7.2 + 0.35} (186.61) = 178.65$$

$$I_{ss} = \frac{0.35}{7.2 + 0.35} 186.61 = 8.65$$

$$I_{f7} = \frac{10.15}{10.15 + 24.08} (46.65) = 13.84 \text{ A}$$

$$I_{s7} = \frac{24.08}{10.15 + 24.08} (46.65) = 32.81 \text{ A}$$

$$I_{f11} = \frac{15.95}{15.95 + 61.3} (37.32) = 7.70 \text{ A}$$

$$I_{s11} = \frac{61.3}{61.3 + 15.95} (37.32) = 29.61 \text{ A}$$

$$I_{f13} = \frac{18.85}{18.85 + 77.81} (18.66) = 3.63 \text{ A}$$

$$I_{s13} = \frac{77.81}{77.81 + 18.85} (18.66) = 15.01 \text{ A}$$

	5	7	11	13
I_s	178 ^{8.65}	32.81	29.61	15.01
I_f	8.65 ¹⁷⁸	13.84	7.70	3.63

$$I_{crms} = \sqrt{I_{f1}^2 + I_{f5}^2 + I_{f7}^2 + I_{f11}^2 + I_{f13}^2} = 211.46 \text{ A}$$

$$V_{cpeak} = V_{c1} + V_{c5} + V_{c7} + V_{c11} + V_{c13}$$

$$V_{c5} = I_{f5} X_{c5} = 178 \left(\frac{175.64}{5} \right) = 6.25 \text{ kV}$$

$$V_{c1} = 19.84 \text{ kV}$$

$$V_{c7} = 0.34 \text{ kV}$$

$$V_{c11} = 0.122 \text{ kV}$$

$$V_{c13} = 0.049 \text{ kV}$$

$$V_{cpeak} = 26.6 \text{ kV}$$

$$V_{c(rms)} = \sqrt{V_{c1}^2 + V_{c5}^2 + V_{c7}^2 + V_{c11}^2 + V_{c13}^2}$$

$$= 20.8 \text{ kV}$$

$$\% V_{rms} = \frac{20.8}{19.05} \times 100 = 109\% \quad (\text{limit } 120\%)$$

$$\% I_{rms} = \frac{211.46}{108.46} \times 100 = 194\% \quad (\text{limit } = 180\%)$$

THD before compensation

$$\% \text{ THD} = \frac{\sqrt{\sum I_n^2}}{I_1}$$

$$= \frac{\sqrt{I_5^2 + I_{17}^2 + I_{19}^2 + I_{23}^2}}{I_1}$$

$$= 42.09\%$$

After compensation

$$\% \text{ THD} = \frac{\sqrt{\sum I_{sh}^2}}{I_1}$$

$$= \frac{\sqrt{I_{s5}^2 + I_{s7}^2 + I_{s11}^2 + I_{s13}^2}}{I_{L1}}$$

$$= 10.4\%$$